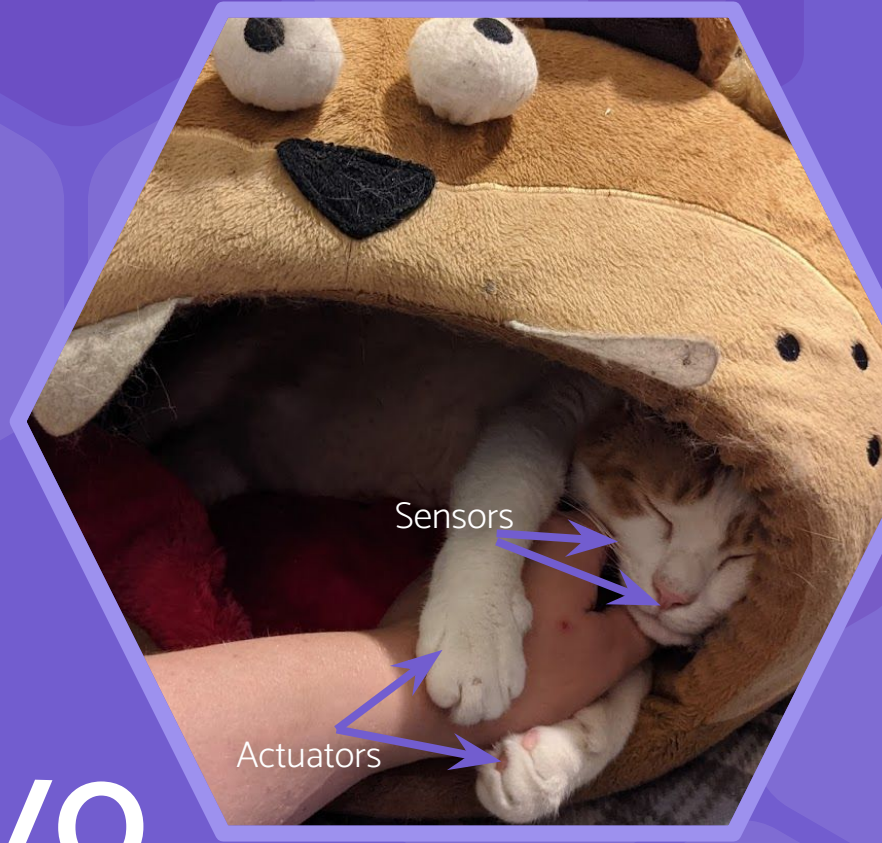


03: Sensors, Actuators, and I/O





Labs start this week!

- Today (Monday) or tomorrow
- *Please* bring your kit if you have it already
- If you want, install the Arduino IDE on your computer (and the SAMD drivers – step 1 of lab)



Homeworks

- Due before class Wednesday and Friday
- First one is out at the end of class
- Smaller, theoretical assignments
 - Typically a short reading and 1-3 questions
- Graded on **good-effort completion**
 - A preview of material taught in lecture
 - You're not expected to know it perfectly
 - If you get stuck, write down why you're stuck and move on



Review


- Circuits are loops through which electricity flows (have a power source and some conductors)
- We learned computations for voltage, current, and power




Interpreting device data sheets

Yellow LED data sheet

What is the actual minimum resistance?

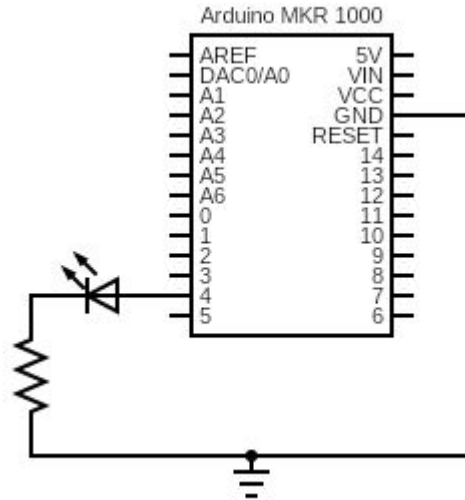

from
data sheet,

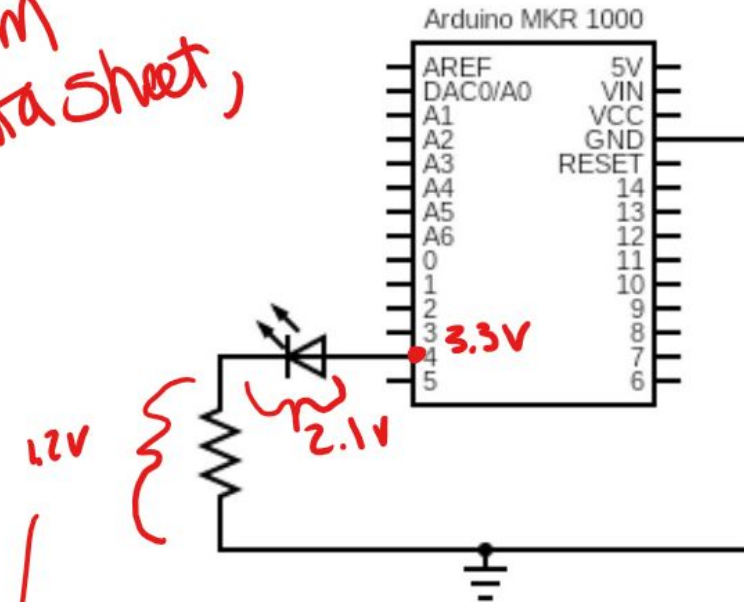

use this voltage to
compute R



Digital devices


Leds are digital **output** devices

Things like push buttons are digital **input** devices

(**When connected correctly**) are driven by or produce a high/low signal




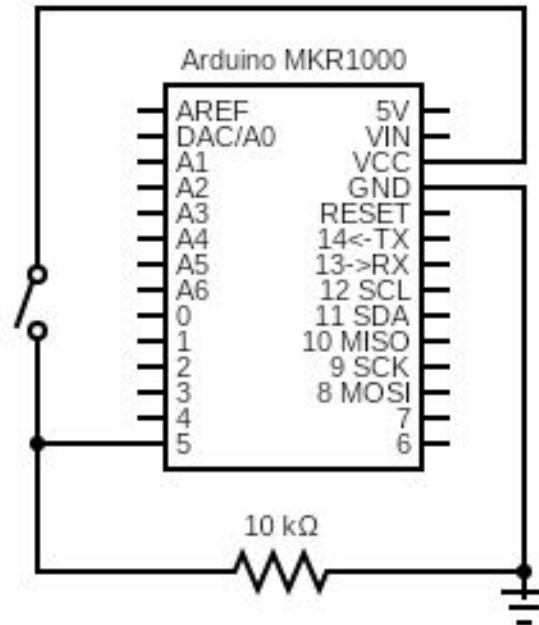Circuit principle: must be closed for electricity to flow




Pin 5 is configured as an input pin (receives electrical signal)

Button not pressed

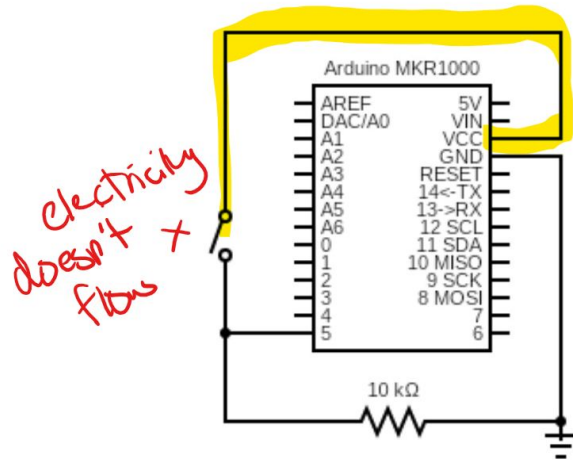


Button pressed

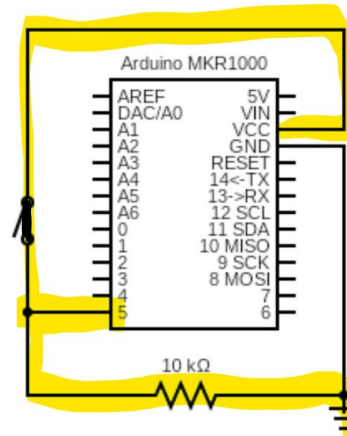

Input components


Your book talks about:

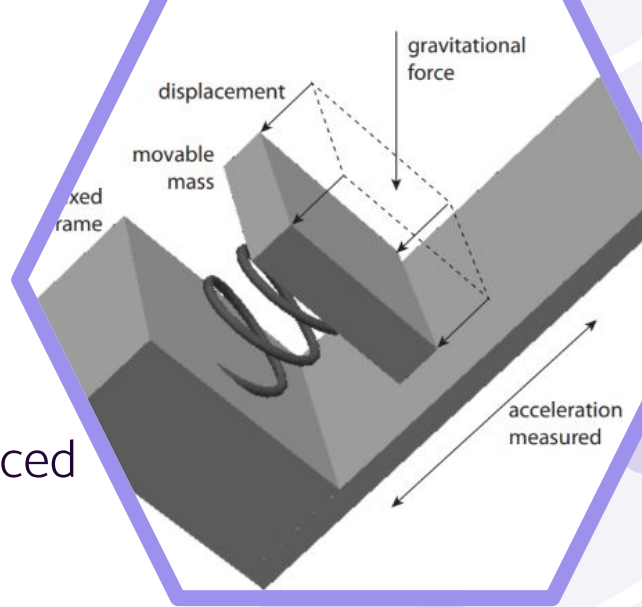- Accelerometers (measure acceleration of displaced mass)
- Anemometers (air flow for velocity)
- GPS (satellite for position)
- Gyroscopes (gimbals and modern)
- Microphones
- Engine controllers, thermometers, cameras, chemical sensors, etc



Other input components in your kits

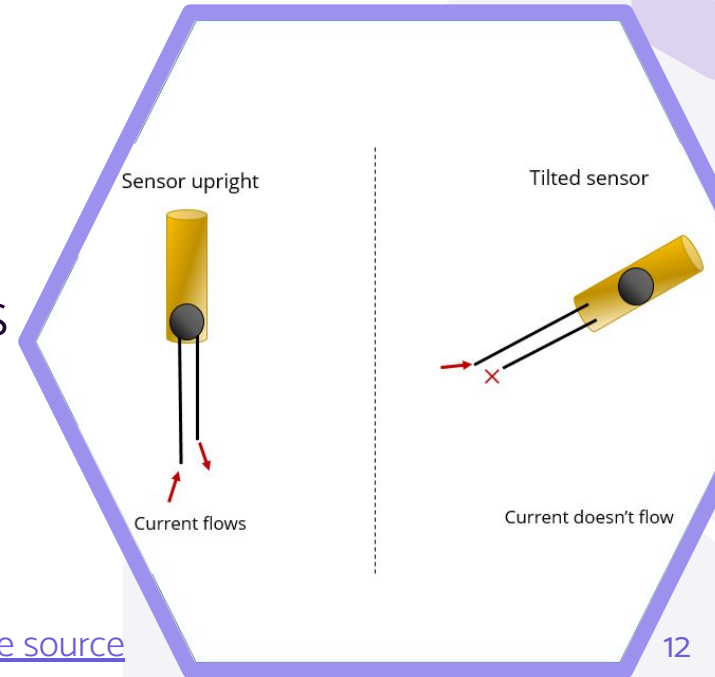- Photoresistor - resistance changes based on light
- Potentiometer - produces voltage based on rotation of the dial
- Tilt sensor - Metal bearing completes circuit




Output components

Your book talks about:

- LEDs
- Motors (DC)

Your kits have:

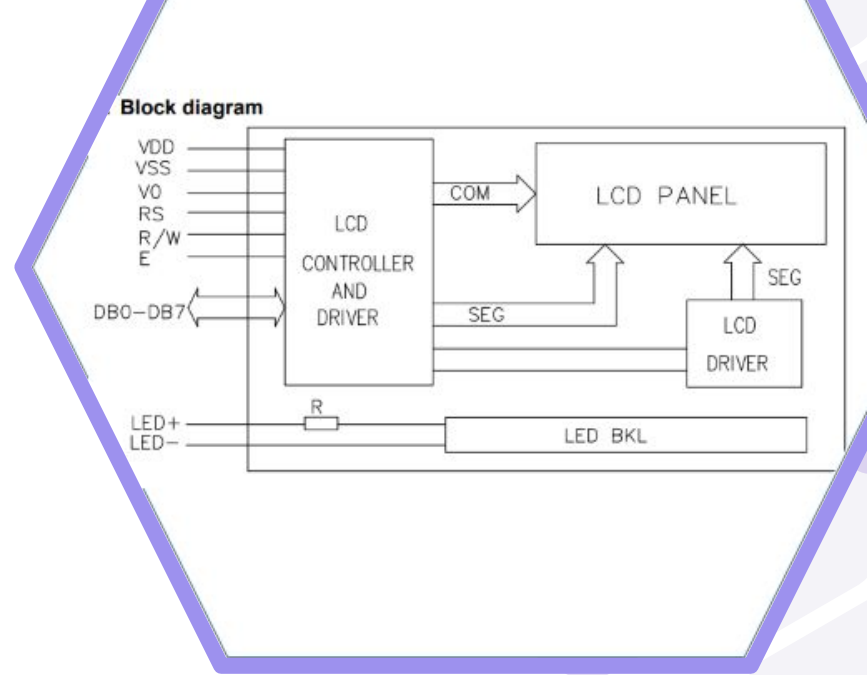- LCD screen (controlled digitally)
- Servo motor (controlled by lengths of high/low pulses)
- Piezo speaker (electricity displaces film to make sound)



[Image source](#)

“

How do you control a DC motor that requires an external power source?


Transistors

Basically an electric switch

Voltage applied to **G**ate connects **D**rain and **S**ource


Come in different types (beyond the scope of this course)

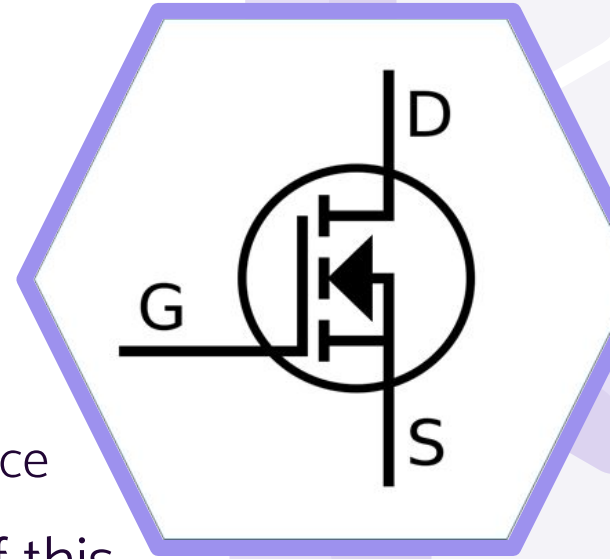The MOSFET transistor in your kits has a minimum gate voltage of 4.2V... what do we do?




Optocouplers

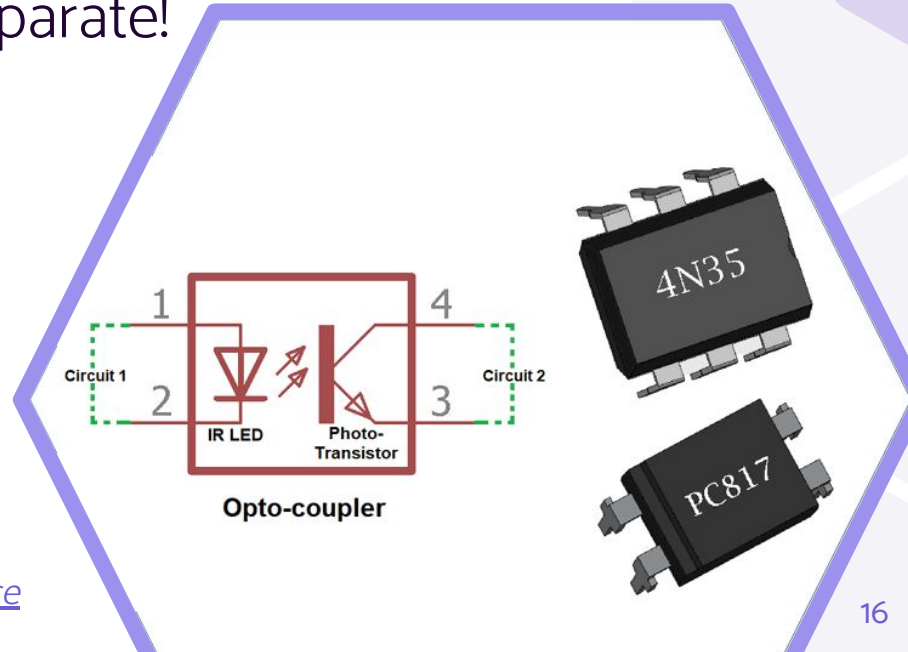- Control one circuit using another, but they are completely electrically separate!




[Image source](#)

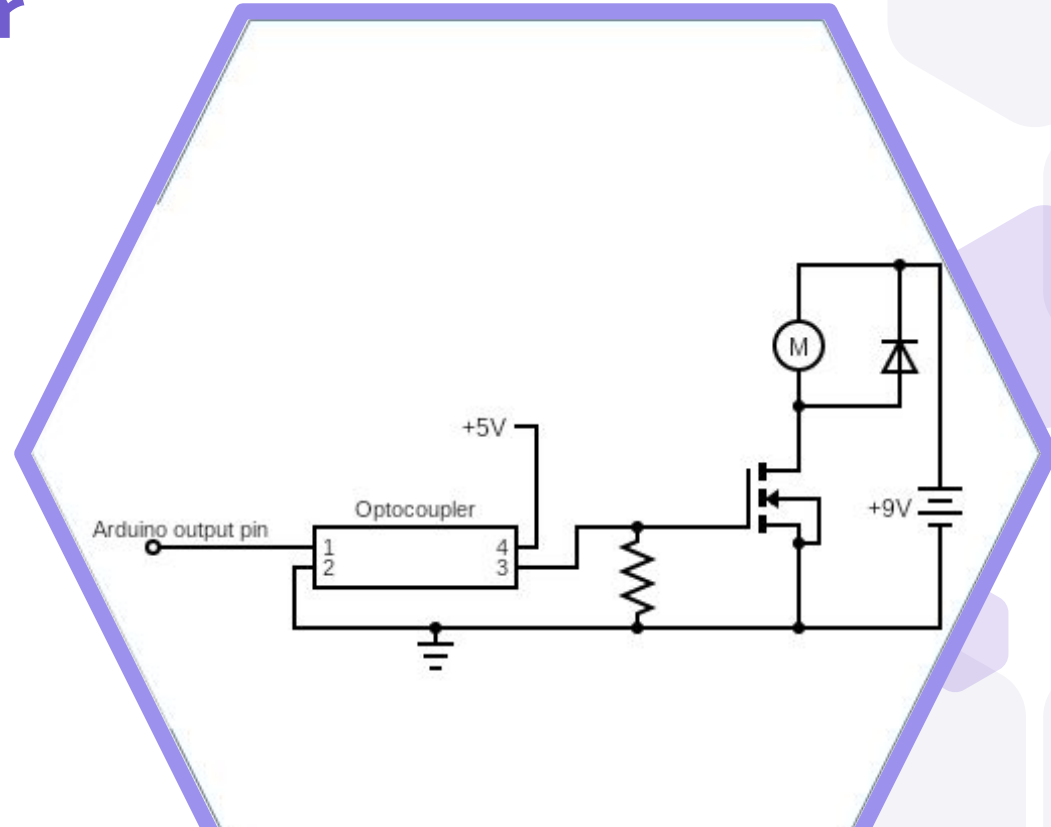Motor driven using mosfet and optocoupler



No voltage from Arduino output pin

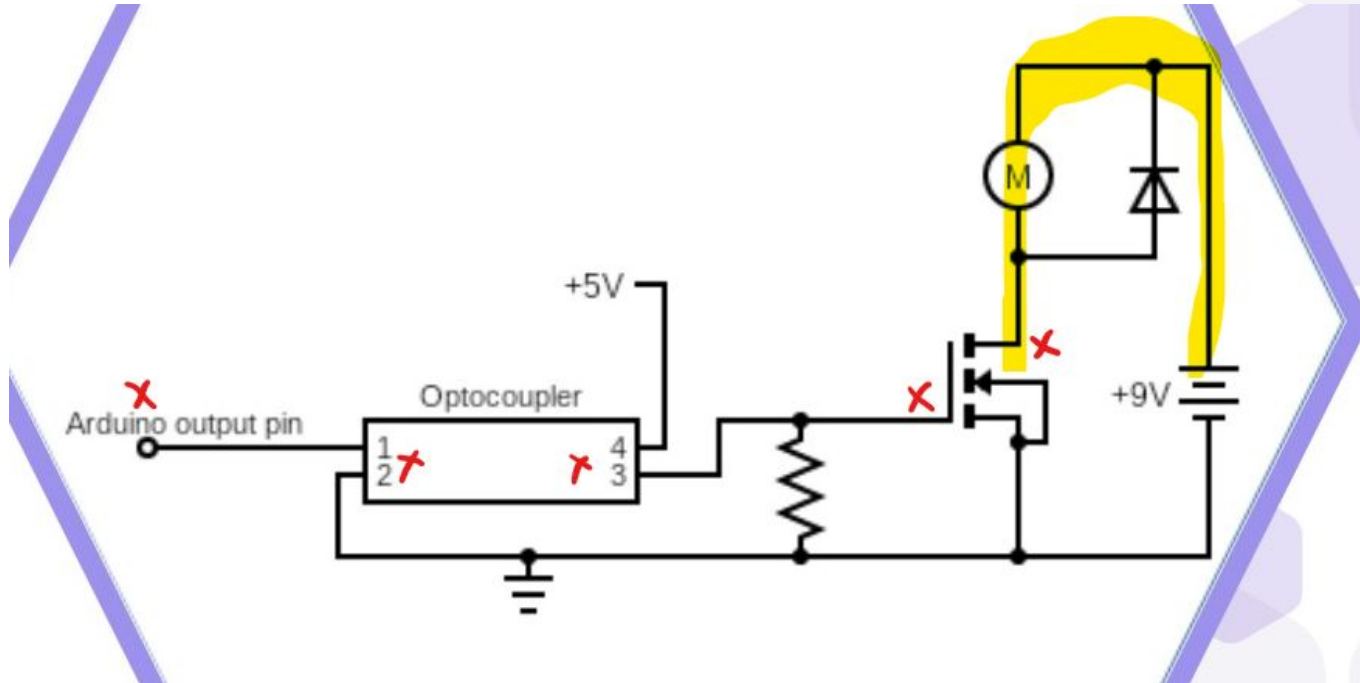

3.3V from Arduino output pin

