


# Nanowire Addressing in the Face of Uncertainty

Eric Rachlin and John E. Savage  
Brown University CS Department  
March 03, 2006


# The Nanowire

- Sets of parallel NWs have been produced.
- Devices will reside at NW intersections.
- We must gain control over individual NWs.


SNAP NWs  
(Heath, Caltech)

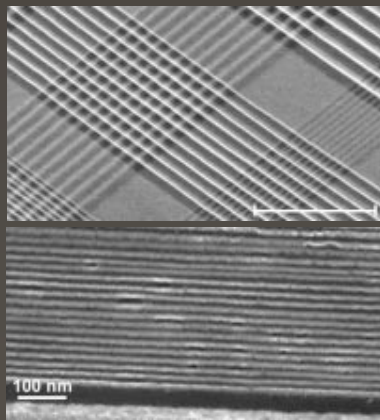

CVD NWs  
(Lieber, Harvard)

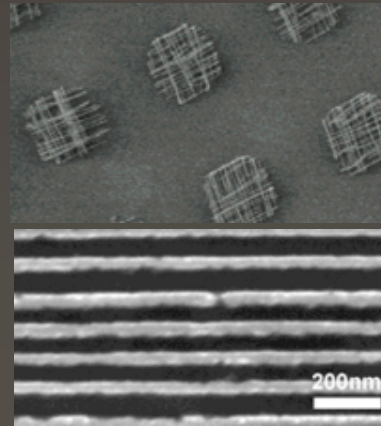

Directed Growth  
(Stoykovich, UW)

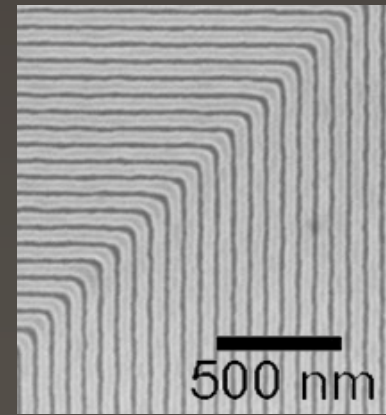


# The Crossbar

The crossbar is currently the most feasible nanoscale architecture.

By addressing individual NWs, we can control programmable molecules at NW crosspoints.

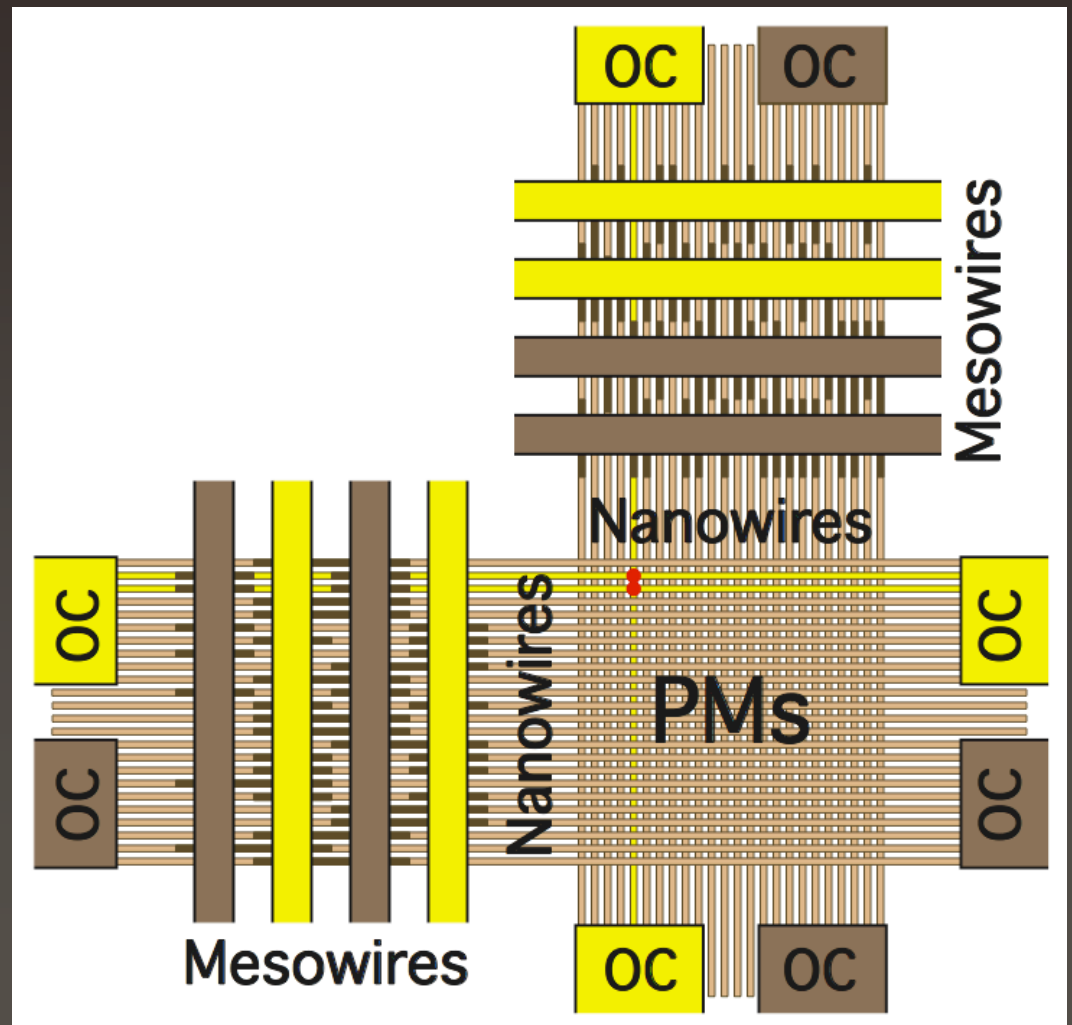Crossbars are a basis for memories and circuits.




# Nanowire Control

- Mesoscale contacts apply a potential along the lengths of NWs.
- Mesoscale wires (MWs) apply fields to across NWs, some of which form FETs.
- NW/MW junctions can form FETs using a variety of technologies:
  - ⇒ Modulation-doping
  - ⇒ Random Particle deposition
  - ⇒ Masking NWs with dielectric material

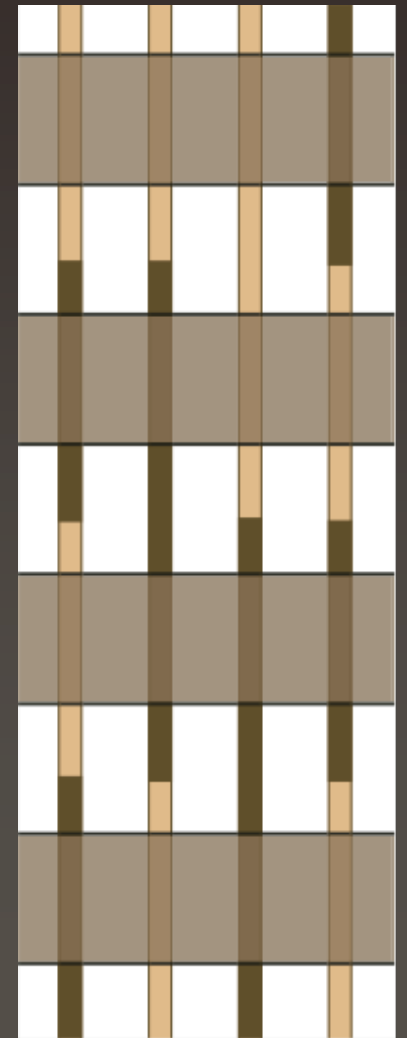
# Simple NW Decoders

- A potential is applied along the NWs.
- $M$  MW inputs control  $N$  NW outputs. Each MW controls a subset of NWs.
- When a MW produces a field, the current in each NW it controls is greatly reduced.
- Each MW “subtracts” out subsets of NWs. This permits  $M \ll N$ .
- Decoders are assembled stochastically and become difficult to produce as  $N$  is large.



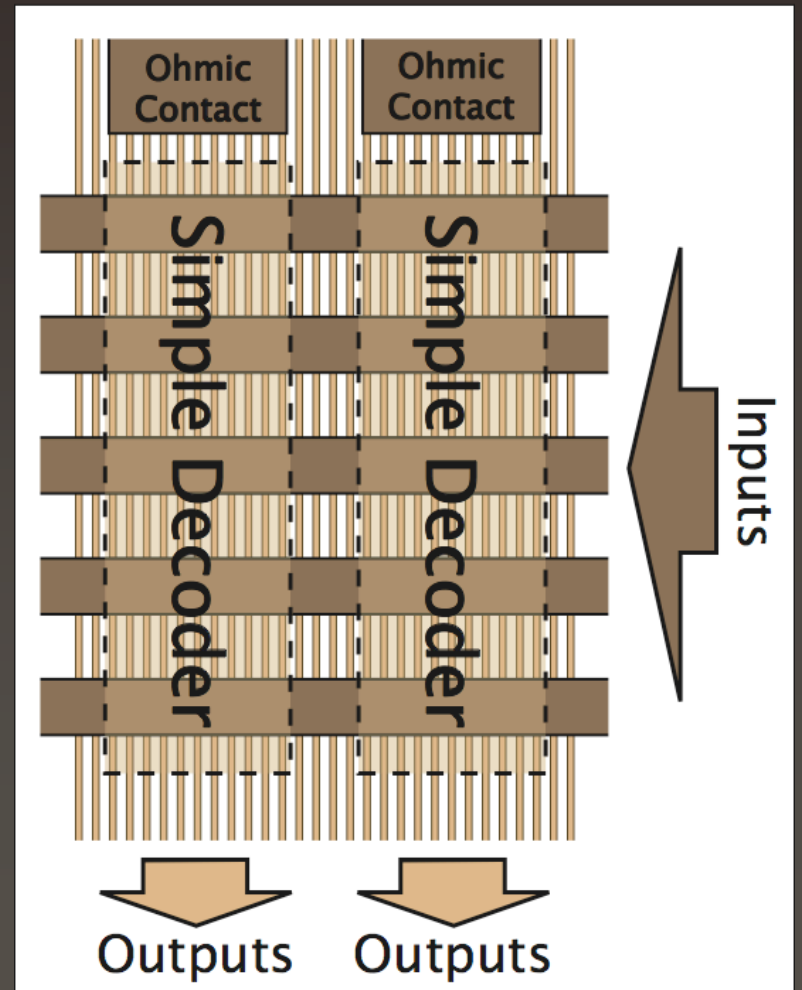
# Composite Decoders

- A composite decoder uses multiple simple decoders to control many NWs.
- The simple decoders share MW inputs.
- This space savings allows for mesoscale inputs.


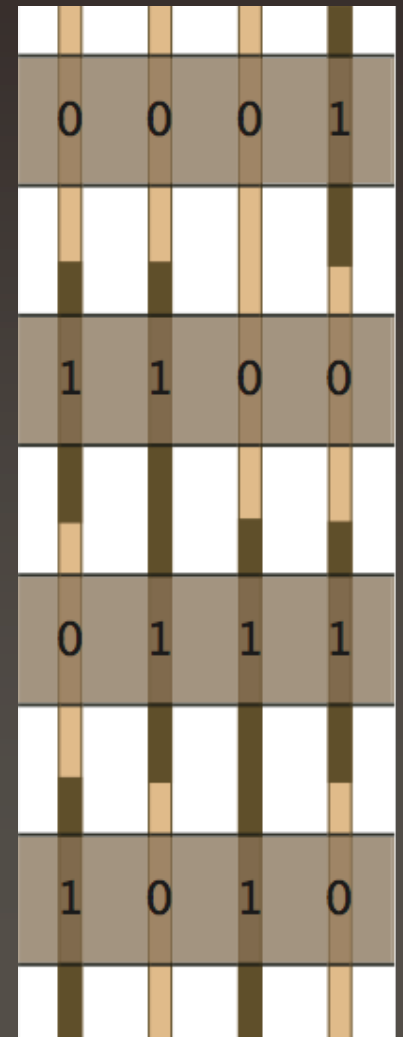
# Binary Codewords

- In a NW decoder, we associate an  $M$ -bit codeword,  $c_i$ , with each NW,  $n_i$ .
- The  $j^{\text{th}}$  MW controls the  $i^{\text{th}}$  NW if and only if the  $j^{\text{th}}$  bit of  $c_i$ ,  $c_{ij}$ , is 1.
- Given the  $M$ -bit decoder input,  $A$ ,  $n_i$  carries a current if and only if  $A \cdot c_i = 0$ .
- Codewords are assigned stochastically.
- Control over codewords is an important way to compare decoding technologies.



# Codeword Interaction


- If  $c_{bj} = 1$  where  $c_{aj} = 1$ ,  $c_a$  **implies**  $c_b$ . Inputs that turn off  $n_a$  turn off  $n_b$ .
- A set of codewords,  $S$ , is **addressable** if some input turns off all NWs not in  $S$ .
- $S = \{c_i\}$  is addressable if and only if no codeword implies  $c_i$ .  $S$  is addressed with input  $A = \overline{c_i}$ .

0	0	0	1
1	1	0	0
0	1	1	1
1	0	0	0


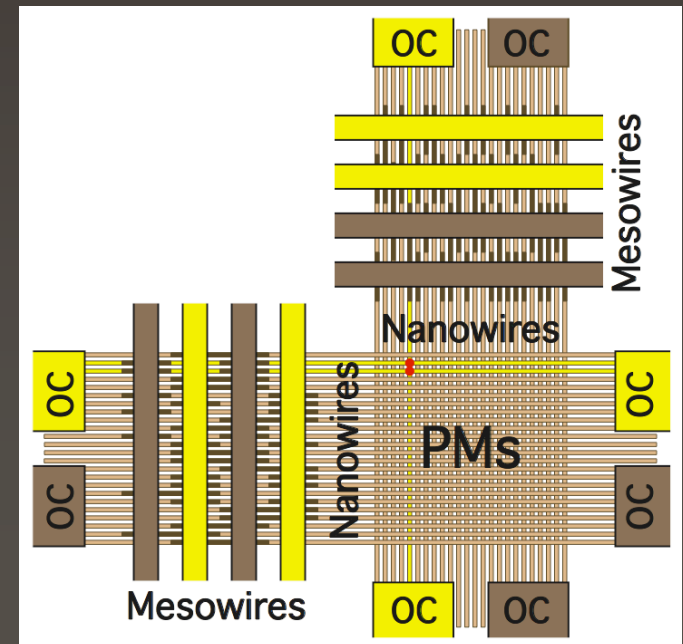
# Decoders for Memories

- A  $B$ -bit memory maps  $B$  addresses to  $B$  disjoint sets of storage devices.
- A  $D$ -address memory decoder addresses  $D$  disjoint subsets of NWs.
- Equivalently, the decoder contains  $D$  addressable codewords.



# Decoders for Circuits


- A MW **uniquely controls** a NW if it controls only that NW.
- In a circuit with  $D$  inputs, we wish to turn on arbitrary subsets of the inputs.
- A  **$D$ -address circuit decoder** addresses arbitrary subsets of  $D$  NWs.
- Each of the  $D$  NWs must be uniquely controlled by some MW.

# Imperfect Control

- Our binary model is accurate if each MW provides good control.
- Realistically, some MWs may only partially turn off some NWs.
- Also, some MWs may occasionally fail to control some NWs.
- Our decoders must be fault-tolerant!
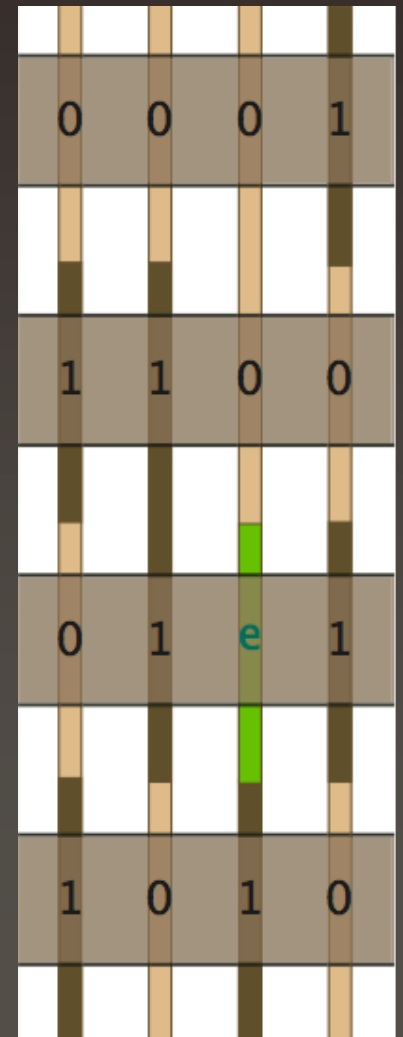
# Ideal Decoders with Errors

- To apply the ideal model to real-world decoders, consider binary codewords with random **errors**.
- If  $c_{ij} = e$ , the  $j^{\text{th}}$  MW increases  $n_i$ 's resistance by an unknown amount.
- Consider input  $A$  such that the  $j^{\text{th}}$  MW carries a field. A functions reliably if a MW for which  $c_{ik} = 1$  carries a field.



# Balanced Hamming Distance

1	0	1	0	1	0	1	0	1	0	1	0
0	1	1	0	0	1	1	0	0	1	1	0
0	0	0	0	0	0	0	0	0	0	0	0

- Consider two error-free codewords,  $c_a$  and  $c_b$ . Let  $|c_a - c_b|$  denote the number of inputs for which  $c_{aj} = 1$  and  $c_{bj} = 0$ .
- The balanced Hamming distance (BHD) between  $c_a$  and  $c_b$  is  $2 \cdot \min(|c_a - c_b|, |c_b - c_a|)$ .
- If  $c_a$  and  $c_b$  have a BHD of  $2d + 2$  they can collectively tolerate up to  $d$  errors.

# Fault-Tolerant Random Particle Decoders

- In a particle deposition decoder,  $c_{ij} = 1$  with some fixed probability,  $p$ .
- If each pair of codeword has a BHD of at least  $2d + 2$ , the decoder can tolerate  $d$  errors per pair.
- This holds with probability  $> 1 - f$  when

$$M > \frac{(d + (d^2 + 4 \ln(N^2/f))^{1/2})^2}{4p(1 - p)}$$

# Conclusion

- Stochastically assembled decoders can reliably control NWs even if errors occur.
- Our decoder model applies to many viable technologies. It provides conditions that a decoder must meet.
- The requirement on circuit decoders suggests an impending IO-challenge.